
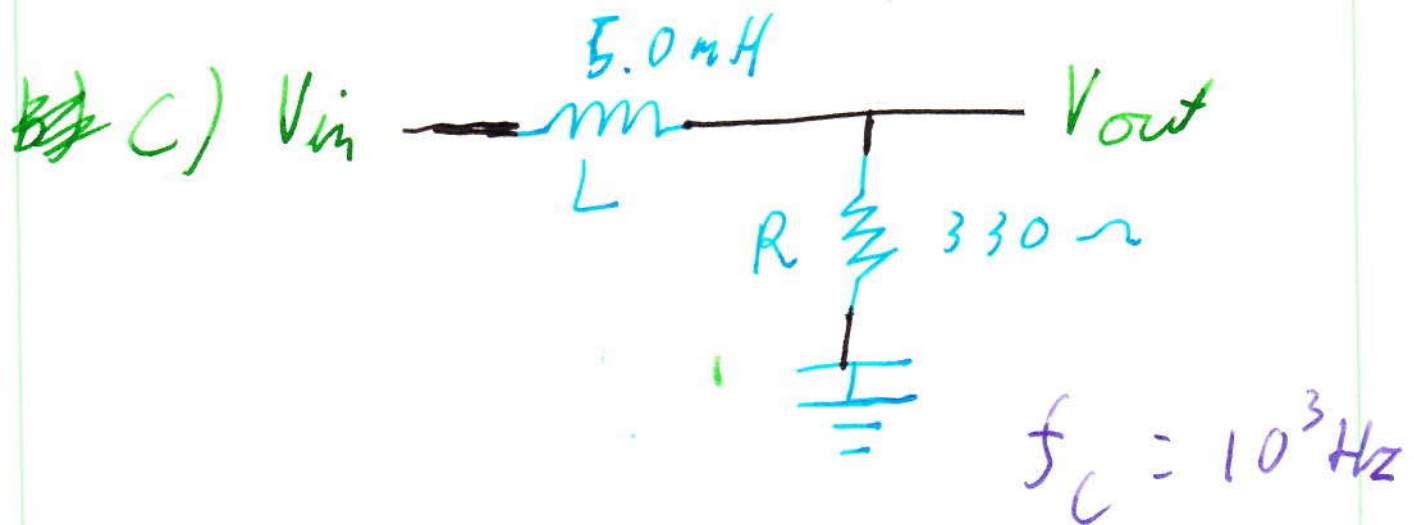


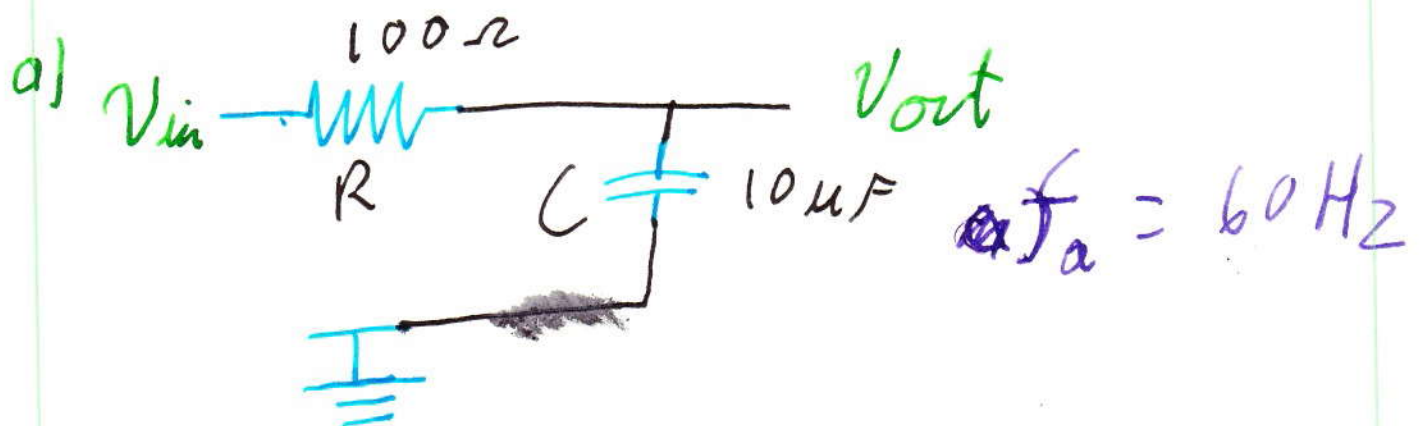3.) Determine the output  $V_{out}$  of each filter in Figure 18-40 at the specified frequency when  $V_{in} = 10V$ .



a)

$$V_{out} = \frac{X_C}{\sqrt{R^2 + X_C^2}} V_{in}$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi (60)(10 \times 10^{-6})}$$

$$V_{out} = \frac{2.6526 \times 10^2}{\sqrt{(100)^2 + (2.6526 \times 10^2)^2}} 10$$

$$V_{out} = 9.3572$$

$$V_{out} = 9.4 \text{ V}$$

c)

$$X_L = f 2\pi L$$

$$X_L = (10^3) 2\pi (5.0 \times 10^{-3})$$

$$X_L = 31.416 \text{ } \cancel{\Omega}$$

$$V_{out} = \frac{\cancel{R}}{\sqrt{R^2 + X_L^2}} V_{in}$$


$$V_{out} = \frac{330}{\sqrt{330^2 + (31.416)^2}} (10)$$

$$V_{out} = 9.955 \text{ V}$$

$$V_{out} \approx 10.0 \text{ V}$$

5) For the filter in Figure 18-41, calculate the value of  $C$  required for each of the following critical frequencies:

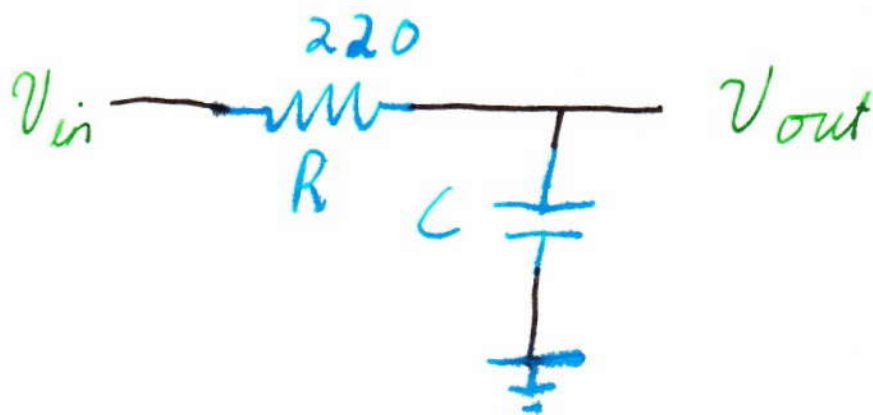b)  $500 \text{ Hz}$     d)  $5 \times 10^3 \text{ Hz}$



$$R = \frac{1}{2\pi fC}$$

$$R 2\pi f = \frac{1}{C}$$


$$\frac{1}{R 2\pi f} = C$$

$$\frac{1}{(220) 2\pi (500)} = 1.4469 \times 10^{-6} F$$



$$\frac{1}{(220)(2\pi)(5000)} = 0.14469 \times 10^{-6} F$$

b)  $1.4 \mu F$   
d)  $0.144 \mu F$

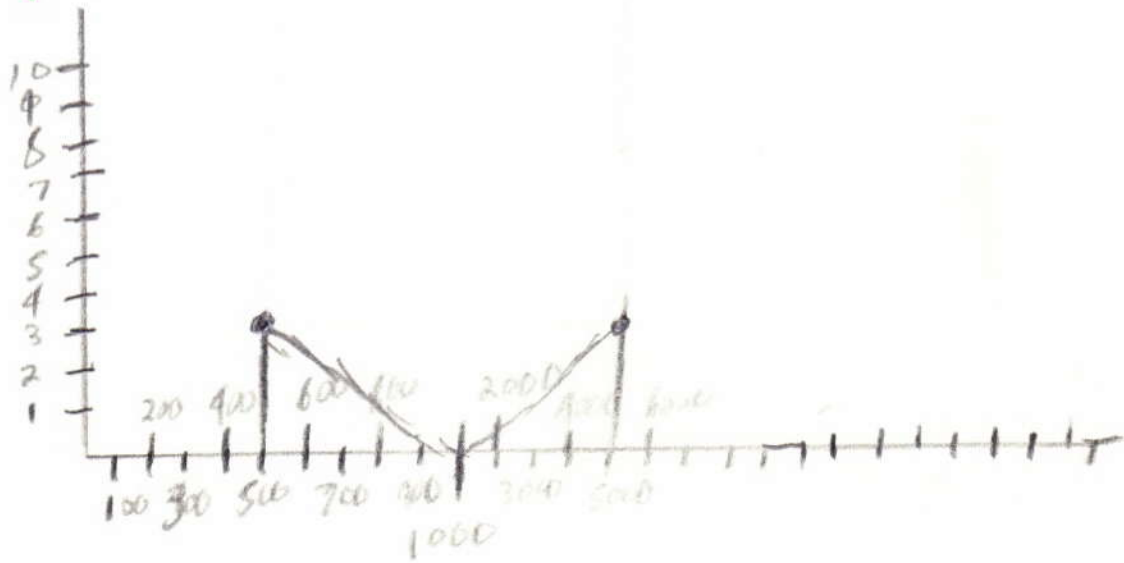7) Draw a Bode ~~plot~~ plot of the magnitude for each part of problem 5.



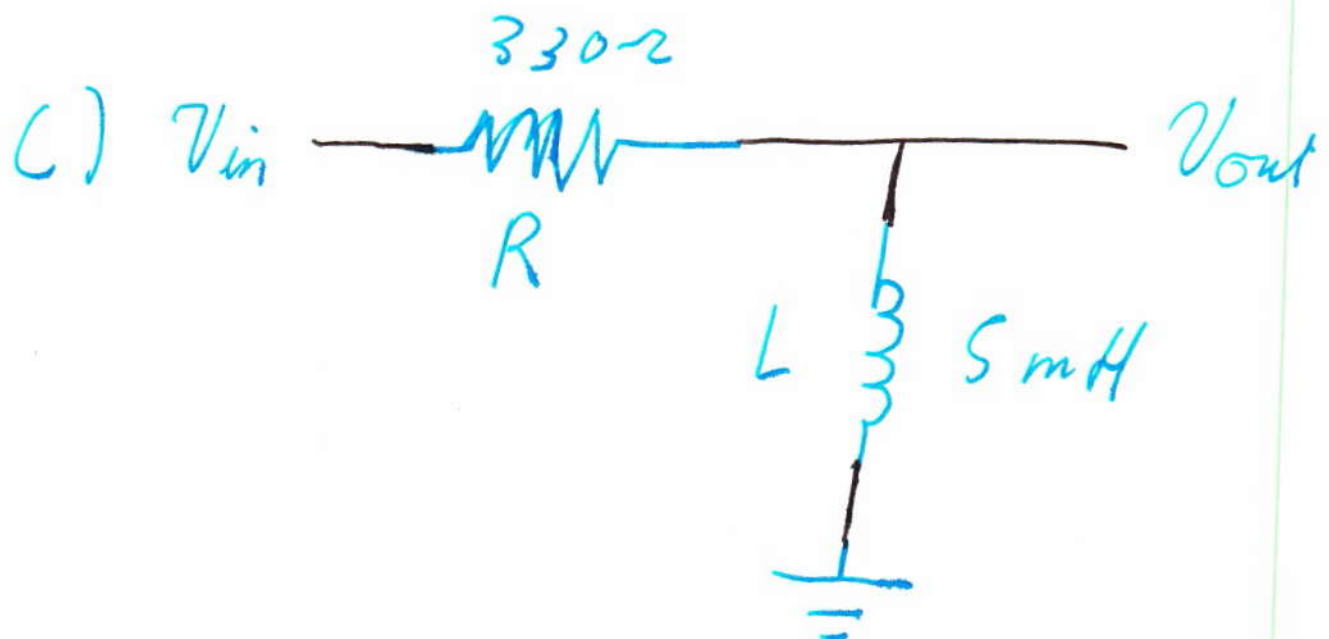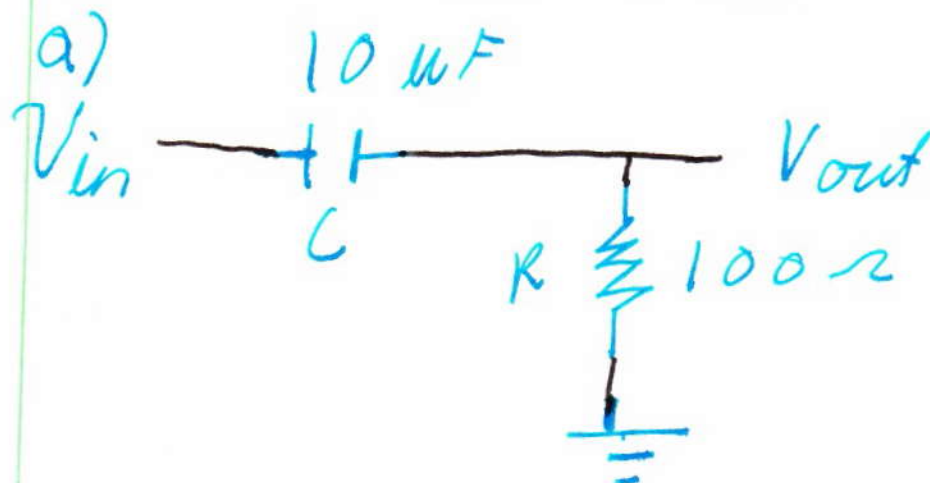16) ~~a)~~ What is  $f_c$  for each filter in Figure 18-43? Determine the output voltage at  $f_c$  in each case ( $V_{in} = 10\text{ V}$ ).





$$a) R = \frac{1}{2\pi fC}$$

$$RC 2\pi = \frac{1}{f}$$

$$\frac{1}{RC 2\pi} = f_c$$

$$\left( \frac{1}{(100)(10 \times 10^{-6}) 2\pi} \right) = f_c$$

$$f_c = 1.5915 \times 10^2$$

$$f_c = 159.2$$

$$V_{out} = \frac{100}{\sqrt{(100)^2 + \left( \frac{1}{2\pi f_c} \right)^2}} \cdot 10$$

$$V_{out} = 5.32 \text{ V}$$

$$V_{out} = 7.07095$$



$$c) \quad V_{out} = \frac{X_L}{\sqrt{R^2 + X_L^2}} V_{in}$$

$$R = X_L$$

$$R = 2\pi f L$$

$$\frac{R}{2\pi L} = f_c$$

$$\frac{330}{2\pi(5 \times 10^{-3})} = f_c$$

$$f_c = 10504.22624 \text{ Hz}$$


$$V_{out} = \frac{330}{\sqrt{330^2 + 330^2}} \cdot 10$$

$$V_{out} = 7.0710678 \text{ V}$$


$$V_{out} = 7.1 \text{ V}$$

23) If the coils in Figure 18-46 have a winding resistance of  $r$ , what is the output voltage at resonance when  $V_{in} = 120V$ ?

a)

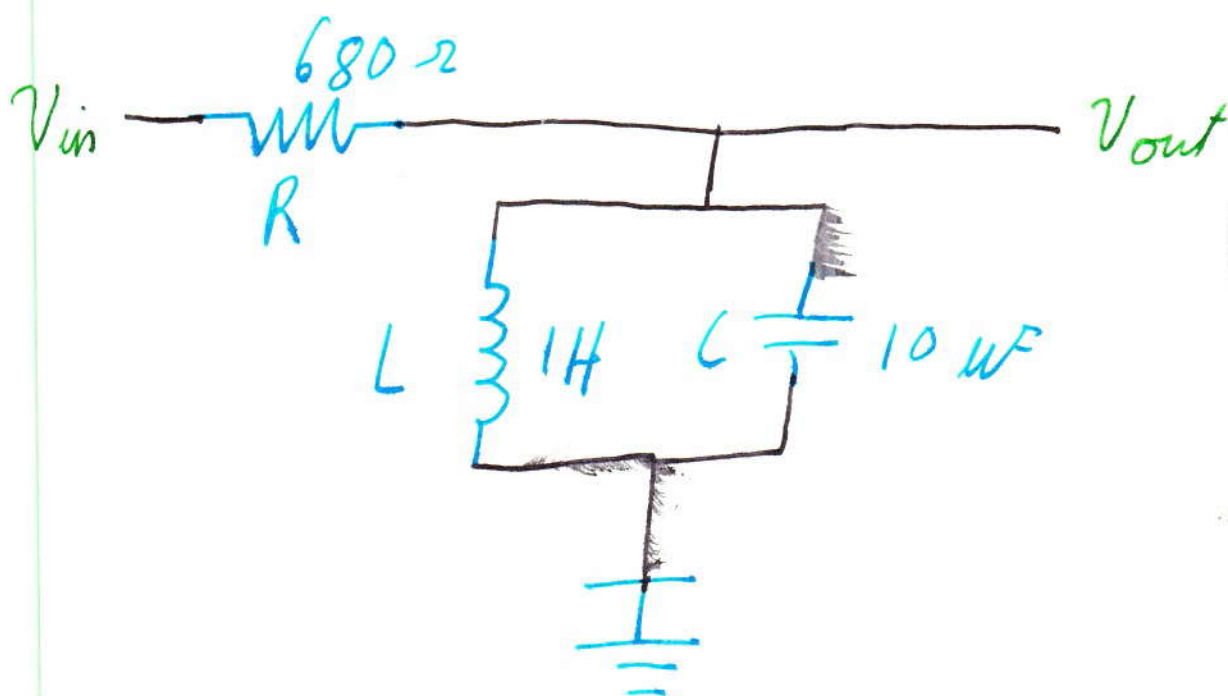

b)

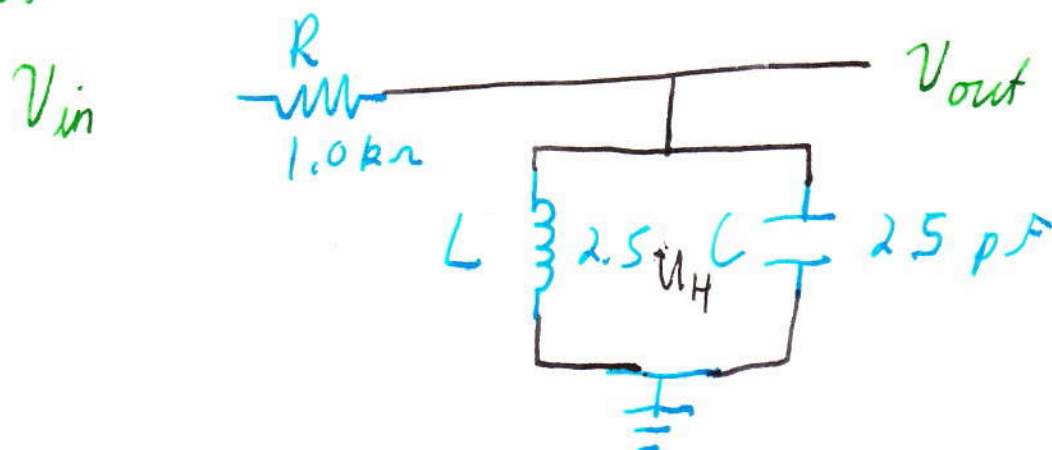

$$f_0 = \frac{\sqrt{1 - \frac{(R\omega^2 L)}{L}}}{2\pi \sqrt{LC}}$$

$$f_0 = \frac{\sqrt{1 - \frac{(4)^2 \times (10 \times 10^{-6})}{1}}}{2\pi \sqrt{(1) \times 10 \times 10^{-6}}}$$

$$2\pi \sqrt{(1) \times 10 \times 10^{-6}}$$

$$f_0 = 50.32518 \text{ Hz}$$

$$f_0 = 50 \text{ Hz}$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_L = 2\pi(50)(1) = 314.1592654 \Omega$$

$$X_C = \frac{1}{2\pi(50)(10 \times 10^{-6})}$$

$$X_C = 318.3098862 \Omega$$

$$Z_L = 4 + 314.159^{2659.} \Omega$$

$$Z_{L||C} = 17349.431 \angle 45.329^\circ$$

$$\frac{Z_{LHC}}{R + Z_{LHC}} \quad V_{in} = V_{out}$$

$$V_{out} = \frac{17349.436 \angle 45.329}{680 + 17349.436 \angle 45.329}$$

$$V_{out} = 116.7391406 \angle 1.55382025^\circ$$

$$V_{out} = 116.7 \angle 1.6^\circ$$

30) Assume you want to reject 60Hz line noise by constructing the parallel resonance band stop filter shown in Figure 18-51.

What size capacitor do you need to complete the filter?

$$X_C = X_L \text{ is required}$$

For resonance

$$\frac{1}{2\pi f C} = 2\pi f L$$

$$2\pi f C = \frac{1}{2\pi f L}$$

$$C = \frac{1}{(2\pi)^2 f^2 L}$$



$$C = \frac{1}{(2\pi f)^2 L}$$

$$C = \frac{1}{(2\pi 60)^2 \times 700 \times 10^{-3}}$$

$$C = 10.0052 \times 10^{-6}$$

$$C = 10 \mu F$$