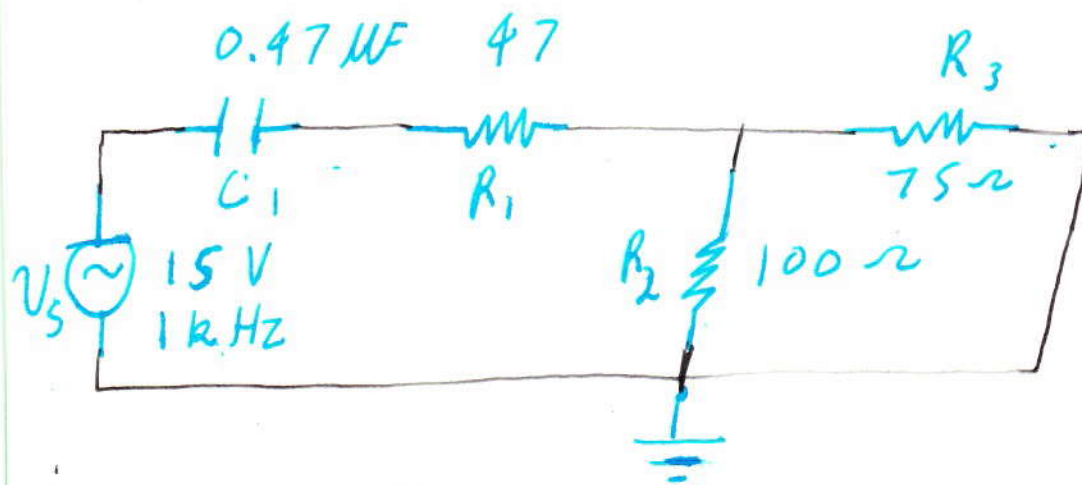


Hw 3

Cpe # 1150

Bruce Liu

62) Determine P_{true} , P_{reactive} , P_{apparent} , and power factor for the circuit in Figure 15-102. Draw the power triangle.



equations

$$P_{\text{apparent}} = i^2 Z$$

$$P_{\text{reactive}} = i^2 X_L$$

$$P_{\text{true}} = i^2 R$$

$$PF = \cos \theta$$

approach

going to find

a thevenin

equivalent circuit

Since the objective
has no element
analysis.

Use i_s and

Z , R , X_L .

$$R_{3112} = \frac{75 \times 100}{100 + 75} = \frac{7500}{175}$$

$$R_{3112} = 42.857$$


$$R_{3112+1} = 89.857 \Omega$$

$$X_C = \frac{-j}{2\pi fC} = \frac{-j}{2\pi (10^3) (4.7 \times 10^{-7})}$$

$$X_C = -338.6275j$$

$$Z_{total} = 89.857 - 338.627j$$

Thevenin equivalent circuit

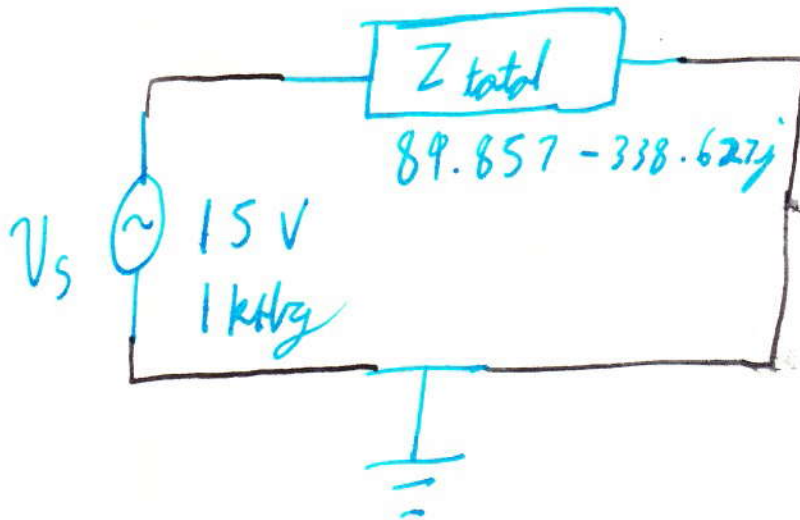

$$V = iZ$$

$$\frac{V}{Z} = i$$

$$\frac{15}{89.857 - 338.627j} = 42.814 \angle 75.138^\circ \text{ mA}$$

$$P_{\text{apparent}} = i_s^2 Z$$

$$P_{\text{apparent}} = (42.814 \times 10^{-3} \angle 75.138^\circ) \times (89.857 - j338.621)$$

$$P_{\text{apparent}} = 0.64222 \angle 75.1386^\circ$$

$$P_{\text{real}} = i_s^2 R$$

$$P_{\text{real}} = (42.814 \times 10^{-3} \angle 75.138^\circ) \times (89.857)$$


$$P_{\text{real}} = 0.164717 \angle 150.277^\circ$$

$$P_{\text{reactive}} = i_s^2 X_C$$

$$P_{\text{reactive}} = (42.814 \times 10^{-3} \angle 75.138^\circ) \times (-j338.621)$$

~~$$P_{\text{reactive}} = 0.6207 \angle 60.277^\circ (-338.621)$$~~
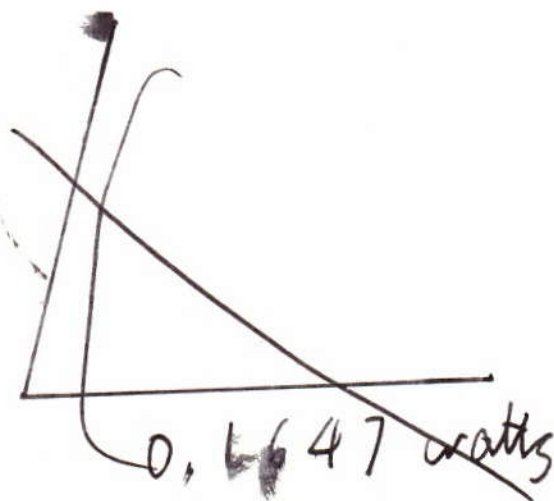
$$P_{\text{reactive}} = 0.6207 \angle 60.277^\circ$$




0.6422


0.6207

75.138°

0.1647

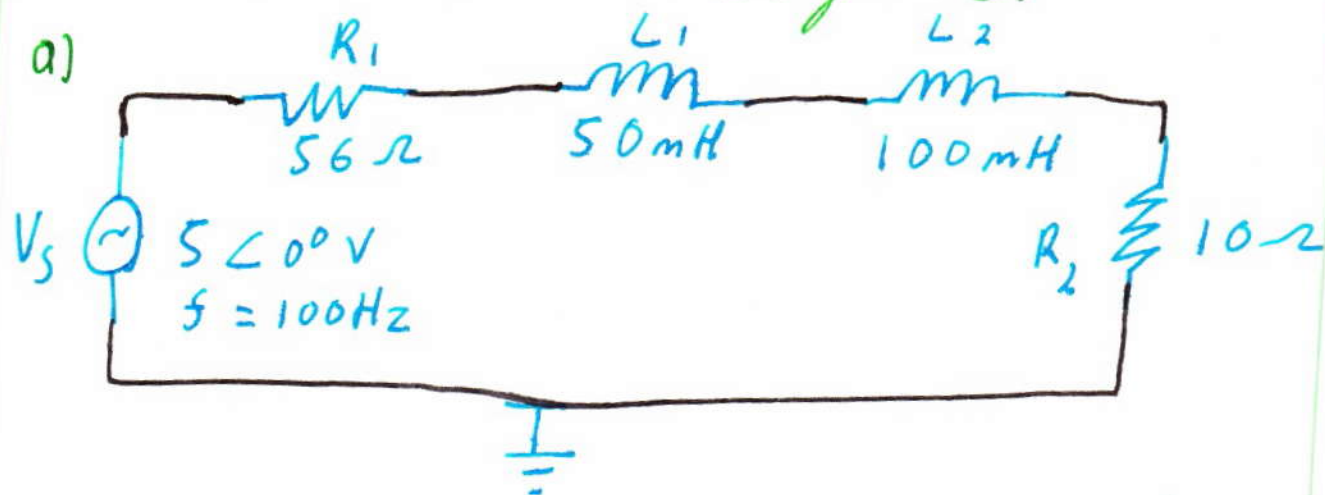4) Determine the impedance magnitude and phase angle in each circuit in Figure 16-59. Draw the impedance diagrams.



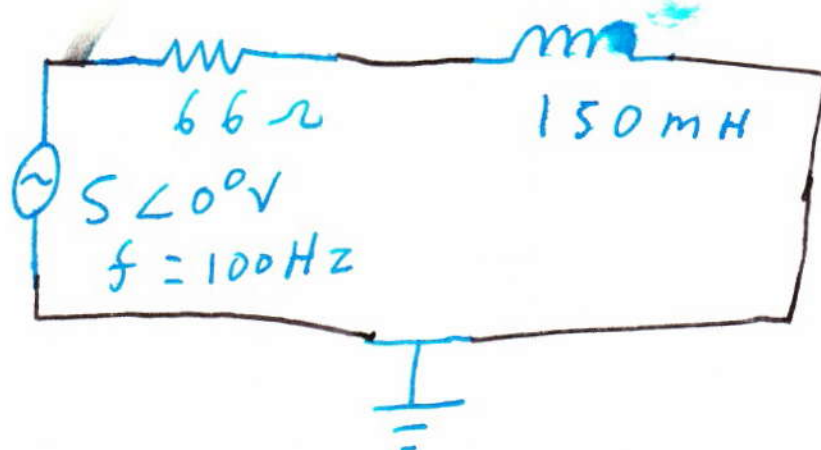


$$2\pi f L = 2\pi(100)(150 \times 10^{-3})$$

$$X_L = 94.247$$

$$Z = 66 + 94.247j$$

$$Z = 115.058 \angle 54.996^\circ$$

b)

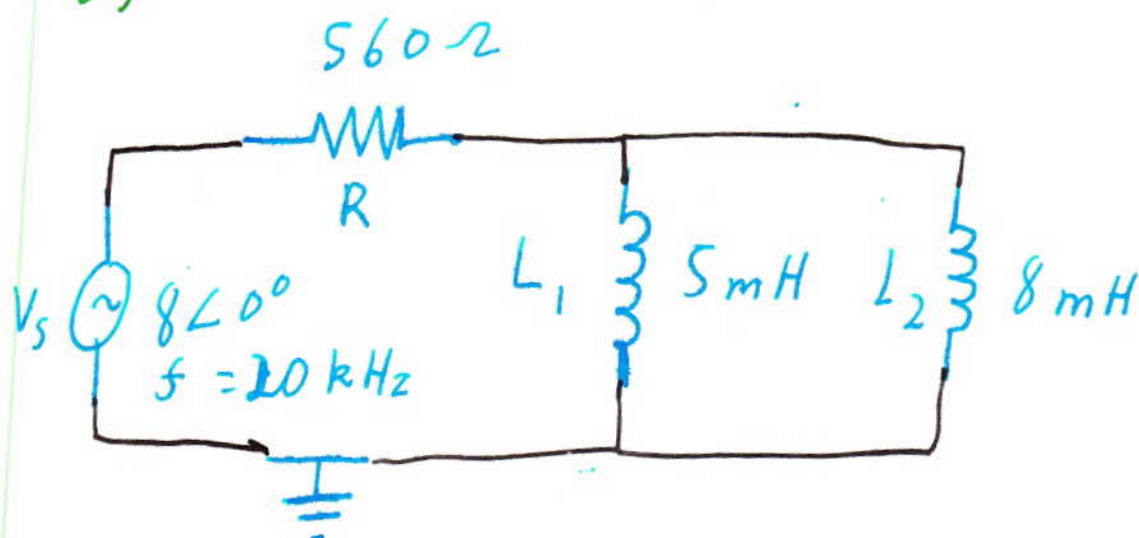

$$\frac{5 \times 10^{-3} \times 8 \times 10^{-3}}{5 \times 10^{-3} + 8 \times 10^{-3}} = L_{\text{Total}}$$

$$L_{\text{Total}} = 3.0769 \times 10^{-3} \text{ H}$$

$$X_L = 2\pi fL$$

$$X_L = 2\pi(20 \times 10^3)(3.0769 \times 10^{-3})$$



$$X_L = 386.5 \times 10^2$$

$$X_L = 386.5 \Omega$$

$$Z = 560 + 386.5j$$

$$Z = 680.427 \angle 34.612^\circ$$

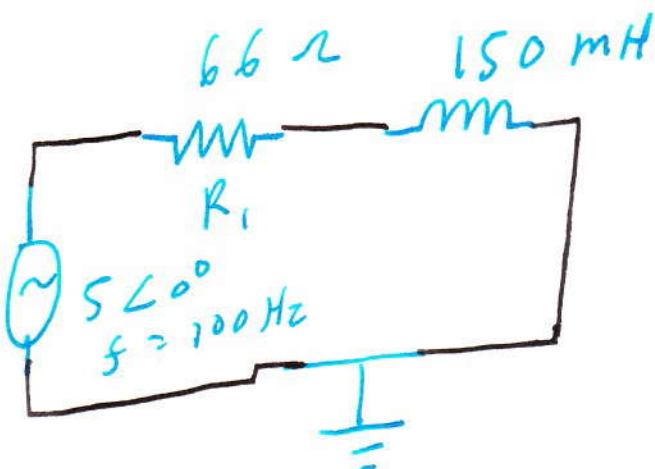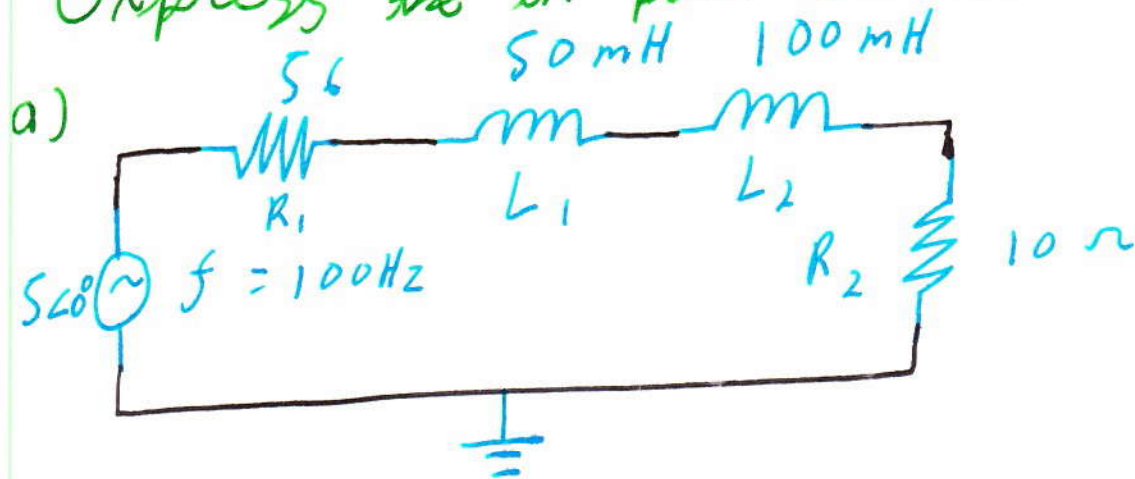11) Calculate the total current in each circuit of Figure 16-59 and express ~~the~~ in polar form.



$$2\pi fL = X_L$$


$$X_L = 2\pi(100)(150 \times 10^{-3})$$

$$X_L = 94.247$$

$$Z = 66 + 94.247j$$

$$\frac{V}{Z} = i \quad i = \frac{5}{66 + 94.247j}$$

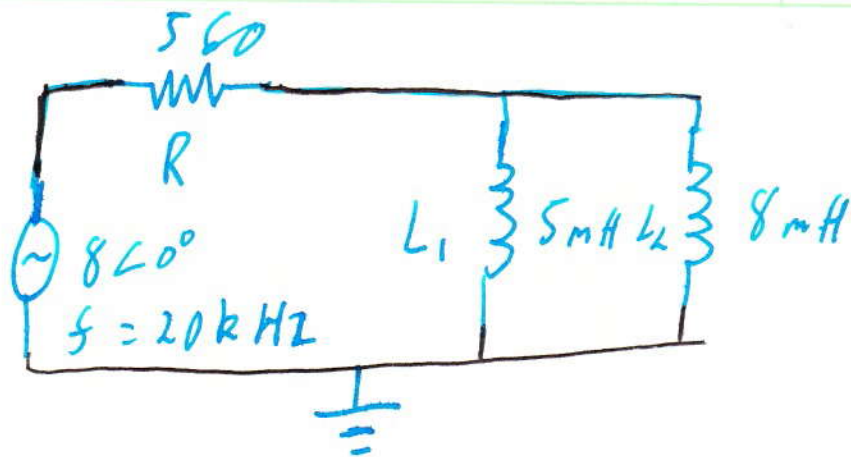all elements have same current series $i = 43.456 \angle -54.996^\circ \text{ mA}$



$$X_{L_1} = 2\pi fL = 2\pi(20 \times 10^3)(5 \times 10^{-3})$$

$$X_{L_1} = 628.318 \, \Omega$$

$$X_{L_2} = 2\pi(20 \times 10^3)(8 \times 10^{-3})$$

$$X_{L_2} = 1005.309 \, \Omega$$

$$\frac{X_{L_1} X_{L_2}}{X_{L_1} + X_{L_2}} = X_{L_{Total}}$$

$$X_L = \frac{628.318 \times 1005.309}{628.318 + 1005.309}$$

$$X_L = 861.001 j \Omega$$

$$Z = 560 + 861.001 j \Omega$$

$$\frac{V}{Z} = i$$

$$\frac{8 \angle 0^\circ}{560 + 860.001 j} = i$$


~~$$i = 9.291 \text{ mA}$$~~

~~$$i = 991.479$$~~

$$i = 552.812 \angle 32.005^\circ$$

17) For the lag circuit in Figure 16-65, determine the phase lag of the output voltage with respect to the input for the following frequencies.

a) 1 Hz d) 10 kHz

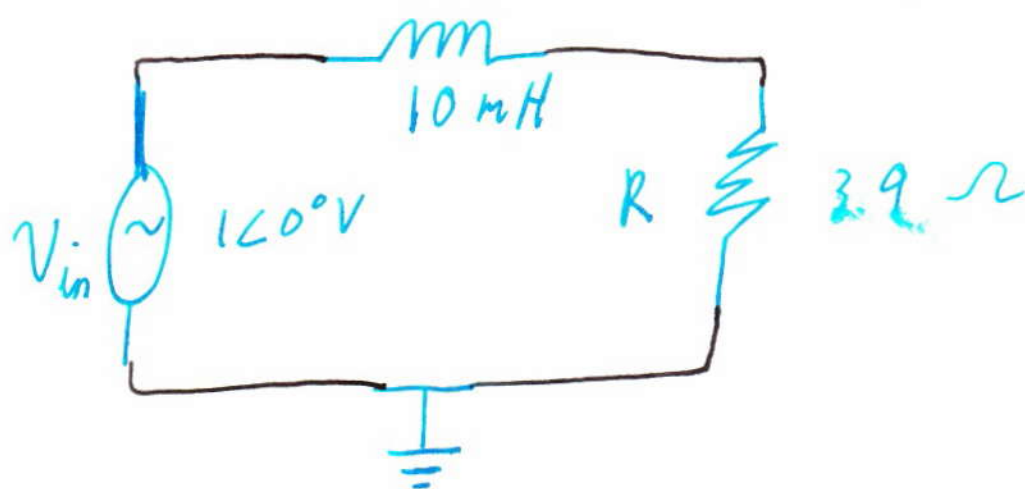

$$X_L = 2\pi fL$$

$$X_L = 2\pi fL$$

$$-\tan^{-1}\left(\frac{X_L}{R}\right) = \theta$$

$$X_L = 2\pi(1)(10 \times 10^{-3})$$

$$X_L = 2\pi(10^{-2})$$

$$-\tan^{-1}\left(\frac{2\pi(10^{-2})}{39}\right) = \theta$$

$$\boxed{-0.092^\circ = \theta \text{ a)}}$$

$$X_L = 2\pi fL$$


$$X_L = 2\pi 10^3 \times 10 \times 10^{-3}$$

$$X_L = 2\pi 10$$

$$-\tan^{-1}\left(\frac{2\pi 10}{39}\right) = \theta$$

$$\boxed{\theta = -58.171}$$

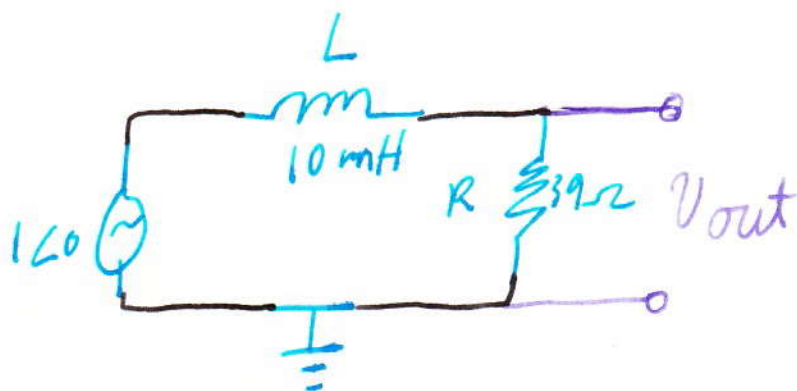19) express V_{out} in Figure 15-66 in polar form for each frequency in problem 17.



b) 100 Hz ✓

c) 10^3 Hz ✓

b)

$$X_L = 2\pi \cancel{(100)} (10 \times 10^{-3})$$

$\cancel{10^{-2}}$

$$X_L = 2\pi$$

$$Z = 39 + 2\pi j$$

$$V_{out} = \frac{39}{39 + 2\pi j} \angle 0^\circ = \frac{R}{Z} V_s$$

$$V_{out} = 0.987 \angle -91.521^\circ$$

c)

$$X_L = 2\pi fL$$

$$X_L = 2\pi \times 10^3 \times 10 \times 10^{-5}$$

$$X_L = 20 \pi$$

$$Z = 39 + 20\pi j$$

$$V_{out} = \frac{39}{39 + 20\pi j} \cdot 1 = \frac{39}{Z} V_s$$

$$V_{out} = 0.527 \angle -58.171^\circ$$

$$28) I_T = i_{R_1} + i_{L_1} + i_{(R_2 + R_3)}$$

$$I_T = (5 + 8.3 + 3) \times 10^{-3}$$

$$I_T = 16.3 \times 10^{-3} \text{ A}$$

cannot be correct
because of inductor.

32) For the circuit in Figure 16-73, determine the following:

a) I_{total}

b) θ


c) V_{R_1}

d) V_{R_2}

e) V_{R_3}

f) V_{L_1}

g) V_{L_2}

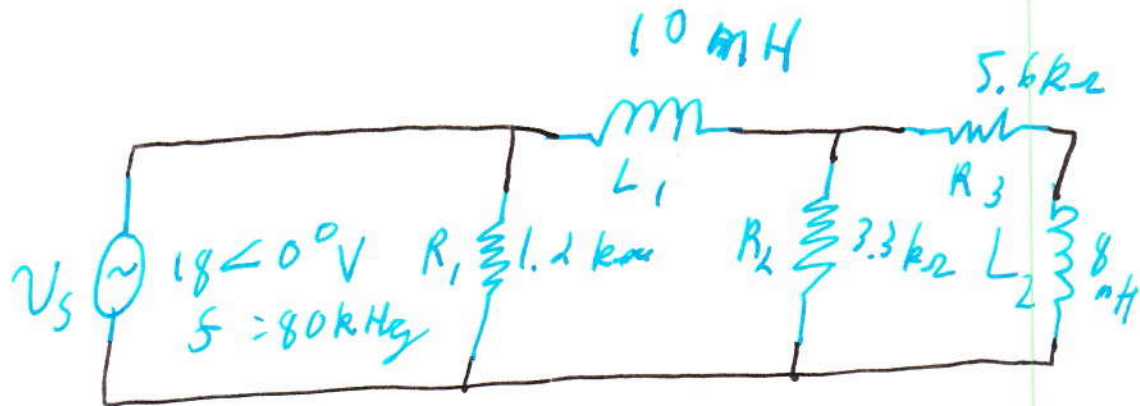

$$X_{L_1} = 2\pi fL$$

$$X_{L_1} = 2\pi(80 \times 10^3)(80 \times 10^{-3})$$


$$X_{L_1} = 2\pi(800)$$

$$X_{L_1} = 5026.548 \text{ j}$$

$$X_{L_2} = 2\pi(80 \times 10^3)(8 \times 10^{-3})$$

$$X_{L_2} = 2\pi 640$$

$$X_{L_2} = 4021.238 \text{ j}$$

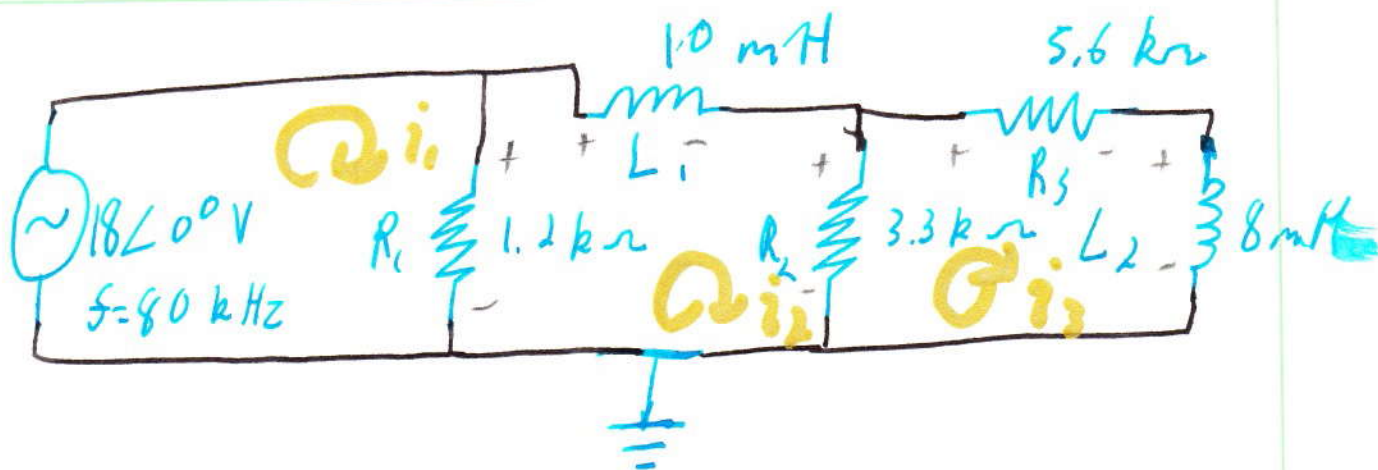

$$0 = i_1 R_1$$

$$0 = (i_1 - i_2) R_1 \quad \text{18}$$

$$0 = (i_2 - i_1) R_1 + (i_2 - i_1) L_1 + (i_2 - i_3) R_2$$

$$0 = (i_3 - i_2) R_2 + (i_3) R_3 + i_3 (L_2)$$

$$\begin{bmatrix} \dot{I}_1 & \dot{I}_2 & \dot{I}_3 \\ R_1 & -R_1 & 0 \\ -R_1 & R_1 + L_1 + R_2 & -R_2 \\ 0 & -R_2 & R_2 + R_3 + L_2 \end{bmatrix} \begin{bmatrix} 18 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 1200 & -1200 & 0 \\ -1200 & (1200 + 5026.548j + 3300) & 0 \\ 0 & 3300 & (3300 + 5600 + 4021.238j) \end{bmatrix} \begin{bmatrix} 18 \\ 0 \\ 0 \end{bmatrix}$$

(3.3 k Ω)

$$\begin{bmatrix} 1200 & -1200 & 0 \\ -1200 & (4500 + 5026.548j) & (3300) \\ 0 & 3300 & 8900 + 4021.238j \end{bmatrix} \begin{bmatrix} 18 \\ 0 \\ 0 \end{bmatrix}$$

$$\dot{I}_1 = 0.01891706 - 0.00204913j$$

$$\dot{I}_2 = 0.00391706 - 0.00204913j$$

$$\dot{I}_3 = -0.00092105 + 0.00117596j$$

$$\dot{I}_1 = 0.19028 \times 10^{-3} \angle -61.823^\circ$$

$$\dot{I}_2 = 4.4207 \times 10^{-3} \angle -27.615^\circ$$

$$\dot{I}_3 = 1.4937 \times 10^{-3} \angle \cancel{128.07^\circ} \angle 128.07^\circ$$

a).

$$i_{total} = i_1 + i_2 + i_3$$

$$i_{total} = (0.19028 \times 10^{-3} \angle -61.823^\circ) + \\ (4.4207 \times 10^{-3} \angle -27.615^\circ) + \\ (1.4937 \times 10^{-3} \angle 128.07^\circ)$$

~~$$i_{total} = 1.9908$$~~

$$i_{total} = 0.19908 \times 10^{-3} \angle 53.004^\circ$$

b) \angle

$$b) 53.004^\circ$$

$$c) V_{R_1} = R_1 (i_1 - i_2)$$

$$V_{R_1} = 1200 (0.19028 \times 10^{-3} \angle -61.823^\circ - 4.4207 \times 10^{-3} \angle -27.615^\circ)$$

$$V_{R_1} = 23.391 \angle 74.929^\circ$$

$$d) V_{R_2} = R_2 (i_2 - i_3)$$

$$V_{R_2} = 3300 (4.4207 \times 10^{-3} \angle -27.615^\circ - 1.4937 \times 10^{-3} \angle 128.07^\circ)$$

~~$$V_{R_2} = 1.918$$~~

$$V_{R_2} = 19.183 \angle -33.685^\circ$$

e)

$$V_{R_3} = R_3 \dot{i}_3$$

$$V_{R_3} = 5000 \times 1.4937 \times 10^{-3} \angle 128.07^\circ$$

$$V_{R_3} = 8.3608 \angle 128.07^\circ$$

f) $V_{L_1} = X_{L_1} \dot{i}_2$

$$V_{L_1} = 5026.548j \times (4.4207 \times 10^{-3} \angle -27.615^\circ)$$

$$V_{L_1} = 22.217 \angle 62.385^\circ$$

2)

$$V_{L_2} = X_{L_2} \dot{i}_3$$

$$V_{L_2} = 4021.236j \times (1.4937 \times 10^{-3} \angle 128.07^\circ)$$

$$V_{L_2} = 6.0037 \angle -141.93^\circ$$

41) Determine P_{true} , P_{reactive} , P_{apparent} and PF for the circuit in Figure 16-73.
Sketch the power triangle.

$$P = iV$$

~~$$V = 18 \angle 0^\circ$$~~

$$V = 18 \angle 0^\circ$$

$$i_{\text{total}} = 0.19908 \times 10^{-3} \angle 53.001^\circ$$

$$P_{\text{true}} = 2.1565 \times 10^{-3}$$

$$P_{\text{reactive}} = 2.8619 \times 10^{-3}$$

$$P_{\text{apparent}} = 3.5834 \times 10^{-3}$$

$$\text{PF} = 53.001^\circ$$

