

## **EET 1150**

- 1. LAB NUMBER:** **6**
- 2. TITLE:** **Thévenin and Norton Theorems  
and Maximum Power Transfer**
- 3. OBJECTIVES:**

After completing this lab, the student will be able to:

1. determine experimentally the parameters of the Thévenin and Norton equivalent circuits,
2. verify the validity of the theorems,
3. verify the validity of the Maximum Power Transfer Theorem.

#### **4. EQUIPMENT:**

METEX MS-9150 Generator  
Oscilloscope  
Experimenter board

#### **5. COMPONENTS:**

- 1 - 10  $\Omega$  ½ watt 5% Resistor
- 2 - 100  $\Omega$  ½ watt 5% Resistor
- 1 - 470  $\Omega$  ½ watt 5% Resistor
- 1 - 510  $\Omega$  ½ watt 5% Resistor
- 1 - 560  $\Omega$  ½ watt 5% Resistor
- 2 - 1000  $\Omega$  ½ watt 5% Resistor
- 4 - 33 nF Capacitor
- 1 - 15 mH Inductor

#### **6. TEXT REFERENCE:**


Circuit Analysis: Theory and Practice (5<sup>th</sup> Edition):  
A.H. Robbins and W.C. Miller

Section 20.3: Thévenin's Theorem – Independent Source  
Section 20.4: Norton's Theorem – Independent Source  
Section 20.6: Maximum Power Transfer Theorem

## 7. PRE-LAB ASSIGNMENT:

Study Fig. 1 and do the following calculations:  
(Attach all your calculations as an Appendix at the end of your team's Report).

Figure 1:

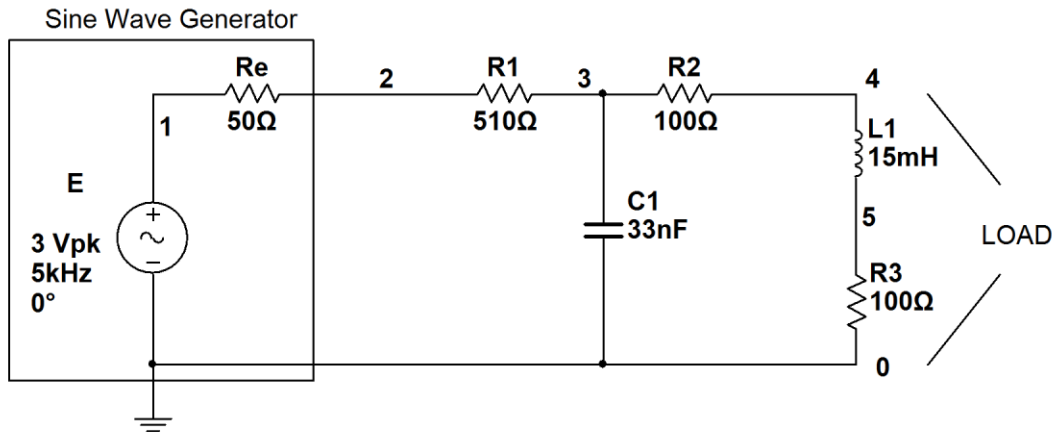

### A – Calculation of $Z_{TH}$ ( $Z_N$ ):

- a) Redraw the circuit with the Load between points “4-0” removed and the source E shorted. Calculate the equivalent impedance  $Z_{TH}$  (or  $Z_N$ ), taking Re into account. Record your result in Table 1.

Table 1:

$Z_{TH}$ ( $Z_N$ )
$\Omega < \quad ^\circ$

### B – Calculation of $E_{TH}$ :

- b) With the Load still removed, and E attached, calculate the voltage (that can be measured) between points “4-0”, that voltage is  $E_{TH}$ . Don't forget to convert E into phasor form with magnitude in RMS. Record your result in Table 2.

Table 2:

$E_{TH}$
$V < \quad ^\circ$

### C – Calculation of $I_N$ :

- c) To calculate the Norton's equivalent current ( $I_N$ ), draw a short between points “4-0” then calculate the current that flows in the short.

Note the direction of this current as it affects the direction of the Norton Current Source. Record your result in Table 3.

Table 3:

$I_N$
mA < °

d) Draw the Thévenin's and Norton's equivalent circuits.

#### **D – Calculation of $R_L$ for Relative Maximum Power:**

e) Look at the result in Table 1 for  $Z_{TH}$  (use rectangular form) to decide if a condition for Absolute Maximum Power can be achieved. If not, calculate the value of the load Resistance  $R_L$  for Relative Maximum Power using the following formula:

$$R_L = \sqrt{R_{TH}^2 + (X_L - X_{TH})^2} \quad (\text{Section 20.6})$$

Table 4:

$R_L$
$\Omega$

### **8. MEASUREMENTS:**

#### **A – Measurement of $E_{TH}$ :**

a) Connect CH1 of the oscilloscope directly to the output of the Sine Wave Generator. Increase the output until the oscilloscope shows a 3 V peak at 5 kHz. This is the no load value of the source E without any loss across Re (50  $\Omega$ ).

b) Build the circuit of Fig. 1 without the load connected between points “4-0”. CH1 is still connected at the output of the Generator (point “2”). Connect CH2 at point “4” to measure the open circuit voltage across the output “4-0”. Record both magnitude (in RMS) and phase of this voltage in Table 5; it is  $E_{TH}$ .

Table 5:

$E_{TH}$
V < °

c) Compare Table 5 to Table 2.

**B – Measurement of  $I_N$  :**

- d) Use a  $10\ \Omega$  sense resistor connected between points “4-0” to simulate a short circuit condition. Connect CH2 to measure the magnitude (convert to RMS) and phase of the voltage across this sense resistor. Calculate the short circuit current, it is  $I_N$ . Record your result in Table 6.

Table 6:

Vsense	$I_N$
mV< °	mA< °

- e) Compare Table 6 to Table 3.

**C – Determination of  $Z_{TH}$  ( $Z_N$ ):**

- f) We cannot measure  $Z_{TH}$  directly, but we can determine it indirectly through the relationship between Thévenin and Norton circuits, that is:

$$Z_{TH} = \frac{E_{TH}}{I_N}$$

- g) Use the results of Tables 5 and 6 to calculate  $Z_{TH}$ .  
Record your result in Table 7

Table 7:

$Z_{TH}$ ( $Z_N$ )
$\Omega$ < °

- h) Compare Table 7 to Table 1.

**D – Compare Original circuit and Thévenin’s Equivalent circuit:**

- i) Add the load to points “4-0” of the original circuit of Fig. 1. Connect CH2 to point “5” and measure the voltage across this resistor (VR3); this voltage will give you the magnitude and phase of the Load Current  $I_L$ . Record your result in Table 8.

Table 8:

VR3	$I_L$
V< °	mA< °

- j) Build the Thévenin’s equivalent circuit using the values in Tables 5 and 7. You must first re-adjust the source E without anything connected to the value

of  $E_{TH}$  then use the available components either in series or parallel to create a simple network with an impedance equal to (or within 5% of)  $Z_{TH}$ .

k) Draw this circuit and build it with the same Load attached. CH1 is still connected at the output of the Generator, CH2 is connected at point “5” to measure new VR3. Record your results in Table 9.

Table 9:

VR3	$I_L$
V< °	mA< °

l) Compare Table 8 to Table 9.

### **E – Relative Maximum Power:**

m) Change the value of R3 to five different values as in Table 10 (including  $R_L$ , we can use the approximate value of  $560\Omega$ ). Use CH2 to determine the magnitude (RMS) of the voltage across this resistor. From these voltages, calculate the Power dissipated in this resistor. Record your results in Table 10.

Table 10:

R3 ( $\Omega$ )	VR3 (V)	P (mW)
100		
200		
$R_L$ (560)		
1000		
2000		

n) Plot a curve showing Power as a function of R3. Does a curve show a maximum point?

## **9. LAB REPORT REQUIREMENT:**

Your team’s Lab Report should contain the followings:

A Cover Page with Lab Number, Lab Title, Team members’ Names and Date.

An Introductory Page with list of Equipment and Components used.

Result Pages with:

**A – Measurement of  $E_{TH}$  :**

Procedure:

(Summarize the main activities that your team did (past tense) in this section).

Results:

Show a copy of Table 5.

Discussions:

- 1) Answer 8 (c).
- 2) Discuss factors that cause the differences in results.

**B – Measurement of  $I_N$  :**

Procedure:

(Summarize the main activities that your team did (past tense) in this section).

Results:

Show a copy of Table 6.

Discussions:

- 1) Answer 8 (e).
- 2) Discuss factors that cause the differences in results.

**C – Determination of  $Z_{TH}$  ( $Z_N$ ):**

Procedure:

(Summarize the main activities that your team did (past tense) in this section).

Results:

Show a copy of Table 7.

Discussions:

- 1) Answer 8 (h).
- 2) Discuss factors that cause the differences in results.
- 3) Explain why we cannot measure  $Z_{TH}$  using a meter like a DMM.

## **D – Compare Original circuit and Thévenin's Equivalent circuit:**

### Procedure:

(Summarize the main activities that your team did (past tense) in this section).

### Results:

Show copies of Tables 8 and 9.

### Discussions:

- 1) Answer 8 (l).
- 2) Discuss factors that cause the differences in results.
- 3) As far as the Load is concerned, are the two circuits equivalent?

## **E – Relative Maximum Power:**

### Procedure:

(Summarize the main activities that your team did (past tense) in this section).

### Results:

Show a copy of Table 10.  
Show the Power vs.  $R_3$  curve

### Discussions:

- 1) Answer 8 (n).
- 2) Instead of using individual  $R_3$ 's, what type of component can we use to have a better (smoother) curve?

## **F – Conclusions:**

- 1) Are the Thévenin and Norton theorems valid? Explain your answer.
- 2) How accurate is the formula for Relative Maximum Power?  
Explain your answer.
- 3) Are all the Lab Objectives met? Explain if some are not.

### Appendix:

Attach all your Pre-Lab calculations.

---